

Register Transfer Language and Micro-Operations

By
Dr. L.Ranathunga

Lecture 5

Digital System Design

- Uses modular approach
- Modules are constructed from
 - Registers
 - Decoders
 - Arithmetic elements
 - Control logics
- Various modules are interconnected with common data path and control paths to form a digital system
- Register operations within the module could define the module


Micro-Operations

- Operations executed on data stored in registers are called micro-Operations
 - Shift data in registers
 - Count data in registers
 - Clear data in registers
 - Load data in registers
- Micro-operations on registers and control will define the internal h/w organization of a computer system
- To decide the operation within computer system as micro-operation, a descriptive language can use

HDL (Hardware Description Language)

MICROOPERATION ...

 An elementary operation performed (during one clock pulse), on the information stored in one or more registers



$$R \leftarrow f(R, R)$$

f: shift, load, clear, increment, add, subtract, complement and, or, xor, ...

ORGANIZATION OF A DIGITAL SYSTEM

- Definition of the (internal) organization of a computer
 - Set of registers and their functions
 - Microoperations set
 - Set of allowable microoperations provided by the organization of the computer
 - Control signals that initiate the sequence of microoperations (to perform the functions)

REGISTER TRANSFER LEVEL

- Viewing a computer, or any digital system, in this way is called the register transfer level
- This is because we're focusing on
 - The system's registers
 - The data transformations in them, and
 - The data transfers between them.

REGISTER TRANSFER LANGUAGE

- Rather than specifying a digital system in words, a specific notation is used, *register transfer language*
- For any function of the computer, the register transfer language can be used to describe the (sequence of) microoperations
- Register transfer language
 - A symbolic language
 - A convenient tool for describing the internal organization of digital computers
 - Can also be used to facilitate the design process of digital systems.




DESIGNATION OF REGISTERS

- Registers are designated by capital letters, sometimes followed by numbers (e.g., A, R13, IR)
- Often the names indicate function:
 - MAR - memory address register
 - PC - program counter
 - IR - instruction register
- Registers and their contents can be viewed and represented in *various ways*
 - A register can be viewed as a single entity:
 - Registers may also be represented showing the bits of data they contain



DESIGNATION OF REGISTERS

 - Designation of a register
 - a register
 - portion of a register
 - a bit of a register
- Common ways of drawing the block diagram of a register



Register Transfer language

- Symbolic notations used to describe the micro-Operation transfers among register is called a Register Transfer language (RTL)
- Convenient way to describe the internal organization and operation of digital systems.
- Computer registers are designated by capital letters. (Sometimes with numbers)
 - EX: MAR - memory address register
 - PC - Program Counter
 - IR - Instruction register



Register Transfer language

- Provides a language for describing the behavior of computers in terms of step-wise register contents
- Provides a formal means of describing machine structure and function
- Is at the "just right" level for machine descriptions
- Does not replace hardware description languages
- Can be used to describe *what* a machine does (an Abstract RTL) without describing *how* the machine does it
- Can also be used to describe a particular hardware implementation (A Concrete RTL)



RTL

- RTL describes the behavior of computers as stepwise transformations on register contents.
- Describe specific computers at the hardware level
- Variables correspond to the hardware registers
- Operations correspond to the hardware logic
- Verilog is becoming the standard design language in industry



REGISTER TRANSFER

- Copying the contents of one register to another is a register transfer
- A register transfer is indicated as

$R2 \leftarrow R1$

In this case the contents of register R2 are copied (loaded) into register R1

- A simultaneous transfer of all bits from the source R1 to the destination register R2, during one clock pulse
- Note that this is a non-destructive; i.e. the contents of R1 are not altered by copying (loading) them to R2



REGISTER TRANSFER...

- A register transfer such as

$R3 \leftarrow R5$

Implies that the digital system has

- the data lines from the source register (R5) to the destination register (R3)
- Parallel load in the destination register (R3)
- Control lines to perform the action



CONTROL FUNCTIONS

- Often actions need to only occur if a certain condition is true
- This is similar to an "if" statement in a programming language
- In digital systems, this is often done via a *control signal*, called a *control function*
 - If the signal is 1, the action takes place
- This is represented as:

$P: R2 \leftarrow R1$

Which means "if $P = 1$, then load the contents of register R1 into register R2", i.e., if $(P = 1)$ then $(R2 \leftarrow R1)$




HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS


Implementation of controlled transfer

$P: R2 \leftarrow R1$

Block diagram

 

Timing diagram

 

- The same clock controls the circuits that generate the control function and the destination register
- Registers are assumed to use *positive-edge-triggered* flip-flops



SIMULTANEOUS OPERATIONS

- If two or more operations are to occur simultaneously, they are separated with commas

$P: R3 \leftarrow R5, MAR \leftarrow IR$

- Here, if the control function $P = 1$, load the contents of R5 into R3, and at the same time (clock), load the contents of register IR into register MAR



RTL

- Instruction transfer from one register to another
 - $R2 \leftarrow R1$
 - Destination \leftarrow Source
 - $R2(H) \leftarrow PC(8-15)$ - Denote a part of register
- Register transfer under conditions
 - If $(p=1)$ then $(R2 \leftarrow R1)$
 - When p is control signal
 - $P: R2 \leftarrow R1$
- Comma is used to separate operations that execute at the same time
 - $P: R2 \leftarrow R1, R3 \leftarrow R1$ - p is control signal




CONNECTING REGISTRS

- In a digital system with many registers, it is impractical to have data and control lines to directly allow each register to be loaded with the contents of every possible other registers
- To completely connect n registers $\rightarrow n(n-1)$ lines $O(n^2)$ cost
 - This is not a realistic approach to use in a large digital system
- Instead, take a different approach
- Have one centralized set of circuits for data transfer - the **bus**
- Have control circuits to select which register is the source, and which is the destination


BUS AND BUS TRANSFER

Bus is a path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations.

 From a register to bus: $BUS \leftarrow R$



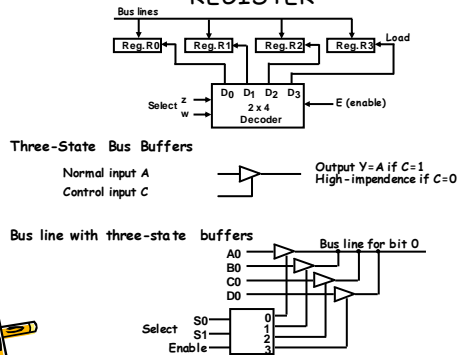TRANSFER FROM BUS TO A DESTINATION REGISTER



BUS TRANSFER IN RTL


- Depending on whether the bus is to be mentioned explicitly or not, register transfer can be indicated as either
- $R2 \leftarrow R1$
- or
- $BUS \leftarrow R1, R2 \leftarrow BUS$

Memory Transfer

- Memory word is symbolized by letter **M**
- Address of the memory location denoted by $M[AR]$
 - AR denotes the address register
 - The data at location given by AR will transfer to DR (Data Register)
 - $DR \leftarrow M[AR]$ - Read operation
 - $M[AR] \leftarrow R1$ - Write Operation


MEMORY (RAM)

- Memory (RAM) can be thought as a sequential circuits containing some number of registers
- These registers hold the *words* of memory
- Each of the r registers is indicated by an *address*
- These addresses range from 0 to $r-1$
- Each register (word) can hold n bits of data
- Assume the RAM contains $r = 2^k$ words. It needs the following
 - n data input lines
 - n data output lines
 - k address lines
 - Read control line
 - Write control line

 

MEMORY TRANSFER

- Collectively, the memory is viewed at the register level as a device, M.
- Since it contains multiple locations, we must specify which address in memory we will be using
- This is done by indexing memory references
- Memory is usually accessed in computer systems by putting the desired address in a special register, the *Memory Address Register (MAR, or AR)*
- When memory is accessed, the contents of the MAR get sent to the memory unit's address lines

 

MEMORY READ

- To read a value from a location in memory and load it into a register, the register transfer language notation looks like this:

$R1 \leftarrow M[MAR]$

- This causes the following to occur
 - The contents of the MAR get sent to the memory address lines
 - A Read (= 1) gets sent to the memory unit
 - The contents of the specified address are put on the memory's output data lines
 - These get sent over the bus to be loaded into register R1

MEMORY WRITE

- To write a value from a register to a location in memory looks like this in register transfer language:

$M[MAR] \leftarrow R1$

- This causes the following to occur
 - The contents of the MAR get sent to the memory address lines
 - A Write (= 1) gets sent to the memory unit
 - The values in register R1 get sent over the bus to the data input lines of the memory
 - The values get loaded into the specified address in the memory

MICROOPERATIONS TYPES

- Computer system microoperations are of four types
 - Register transfer microoperations
 - Arithmetic microoperations
 - Logic microoperations
 - Shift microoperations

Arithmetic Operations

- Add operation
 - $R3 \leftarrow R1 + R2$
- Subtract operation
 - $R3 \leftarrow R1 + R2 + 1 (= R1 - R2 = R3)$
 - R2 is in 1's complement form and by adding 1 it become 2's complement form

ARITHMETIC MICROOPERATIONS

- The basic arithmetic microoperations are
 - Addition
 - Subtraction
 - Increment
 - Decrement
- The additional arithmetic microoperations are
 - Add with carry
 - Subtract with borrow
 - Transfer/Load
 - etc. ...

$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

BASIC SYMBOLS FOR REGISTER TRANSFERS

Symbols	Description	Examples
Capital letters & numerals	Denotes a register	MAR, R2
Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	$R2 \leftarrow R1$
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	$A \leftarrow B, B \leftarrow A$

Logic Operations


- P: $R1 \leftarrow R1 \oplus R2$ - Exclusive OR Operation
- P+Q: $R1 \leftarrow R2$ - OR operation is at control signal
- $R4 \leftarrow R5 \cup R6$ - OR operation on registers
- $R4 \leftarrow R5 \wedge R6$ - And operation on registers
- $R4 \leftarrow R5 \cup R6$ - Nor operation on registers

Shift Micro-Operations


- $R \leftarrow Shl R$ - Shift left register
- $R \leftarrow Shr R$ - Shift right register

SHIFT MICROOPERATIONS

 - There are three types of shifts
 - Logical shift
 - Circular shift
 - Arithmetic shift
- What differentiates them is the information that goes into the serial input
- A right shift operation




- A left shift operation

 


LOGICAL SHIFT

 - In a logical shift the serial input to the shift is a 0.
- A right logical shift operation:



- A left logical shift operation:

 

- In a Register Transfer Language, the following notation is used
 - *shl* for a logical shift left
 - *shr* for a logical shift right

Examples:


- $R2 \leftarrow shr R2$
- $R3 \leftarrow shl R3$

Fetch & Execution Cycle


Fetch cycle:

$MAR \leftarrow PC$
 $INCREMENTER \leftarrow PC$
 $PC \leftarrow INCREMENTER$
 $MBR \leftarrow M[MAR]$
 $IR \leftarrow MBR$
 $CU \leftarrow IR(Opcode)$

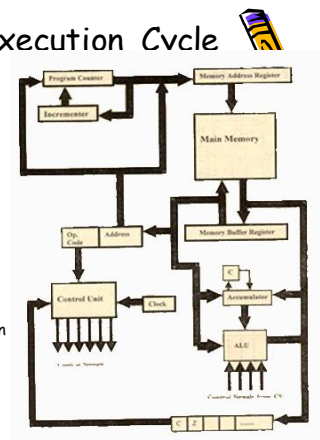If it is a arithmetic operation
Execution Cycle?



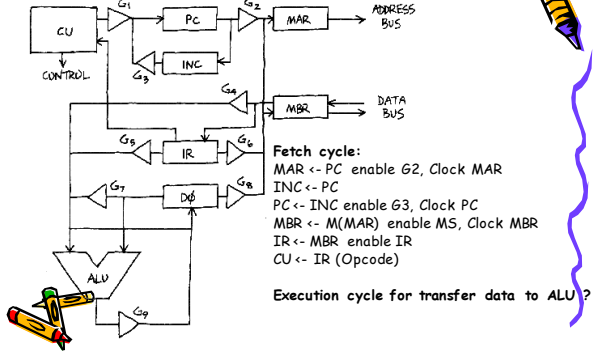Fetch & Execution Cycle with control signals



• Questions?